

Samanta Chandrasekhar Institute of Technology and Mangement

INTERNAL EXAM :1

SEM: 3rd , EE

SUB: CNT

FULL MARK :10

Answer all the questions:

(5*1=5)

- Q1 (i) Draw the Power triangle for R-L series circuits state the Expression for active reactive and apparent power ?
- (II) What is damping in transient analysis ?
- (III) Express the given current $10\angle 60$ degree amp in rectangular Form ?
- (iv) Draw the circuit of Low -Pass R-C circuit ?
- (V) State the expression for Hybrid Parameters ?

Q2. Derive the relationship between phase voltage and line voltage of a balanced 3-Phase star connection ?

(2.5)

Q3. Make a classification of various types of passive electric wave filters and draw their frequency attenuation characteristics ?

(2.5)

INTERNAL EXAM : 2

SEM: 3rd , EE

SUB: CNT

FULL MARK :10

Answer all the questions:

(5*1=5)

Q1 (i) Define Resonance .What is condition for resonance in R-L-C Series circuit ?


(II) Write down the two advantages of active filter over passive filter ?

(III) Define Reluctance ?How is it analogous to electric circuit ?

(iv) Define Time Constant in R-L circuit ?


(V) Define Co-efficient of coupling ?

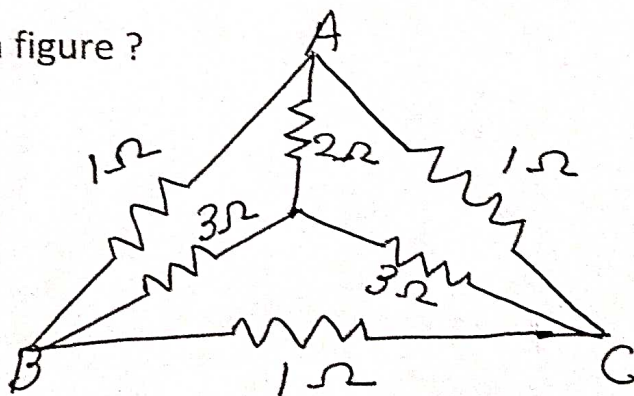Q2. Compute the network resistance of the terminals B and C in the given figure ?



(2.5)

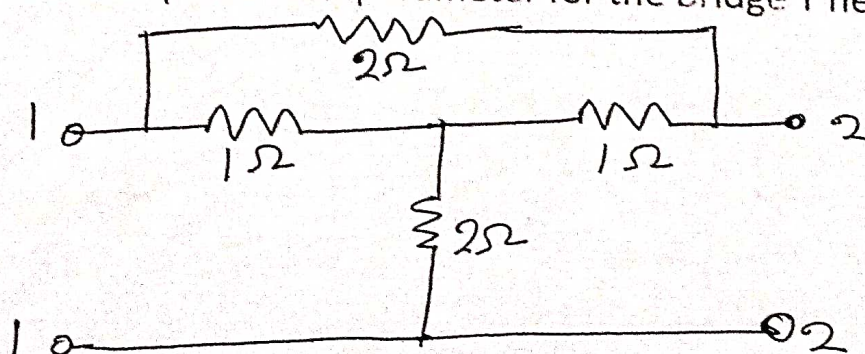Q3. Derive open circuit parameter for the Bridge T network



(2.5)